

# Control a 4-Channel Relay Module with ESP32 (Using 3 Relays)

---

## Components Required:

- 1. ESP32 Development Board
- 2. 4-Channel Relay Module
- 3. 3 LEDs
- 4. 3 Resistors (220Ω or 330Ω each for LEDs)
- 5. Jumper Wires
- 6. Breadboard
- 7. External 5V Power Source (if required for Relay)

## Circuit Diagram and Connections:

ESP32 GPIO Pin	Relay Module IN Pin
GPIO 5	IN1
GPIO 17	IN2
GPIO 16	IN3

## Relay Output Side:

- Connect each relay's **NO (Normally Open)** pin to one end of an **LED + Resistor in series**.
- The other end of the resistor goes to the **GND** of the power supply.
- Common (COM) pin of each relay connects to **+5V (or appropriate supply)** for LEDs.

## Relay Module Power:

- VCC → 5V (ESP32 5V pin or external 5V)
- GND → GND of ESP32
- IN1, IN2, IN3 → GPIO pins (as above)

**Note:**

If relays are powered by an external 5V supply, **connect both ESP32 GND and Relay GND together**.

## Important Notes:

- 1. **Relay Type:**  
Most relay modules are **Active LOW** — setting the GPIO pin to **LOW activates** the relay.
- 2. **ESP32 Power Limit:**  
ESP32's onboard 3.3V cannot drive relay coils — always power the relay module from **5V**.
- 3. **Relay Module Jumper:**  
If your relay has a **JD-VCC jumper**, remove it and power the relay side with a separate 5V

source for safety (especially when switching loads).

#### 4. LED Protection:

Always use **220Ω or 330Ω resistors** in series with LEDs to limit current.

#### 5. Switching Real Devices:

If switching AC appliances — use proper insulation, opto-isolation, and safety measures.

### ESP32 Relay Control Code:

```
#include <Arduino.h>

#define in1 5
#define in2 17
#define in3 16

void setup() {
  pinMode(in1,OUTPUT);
  pinMode(in2,OUTPUT);
  pinMode(in3,OUTPUT);
}

void loop() {
  digitalWrite(in1,LOW);
  delay(1000);
  digitalWrite(in1,HIGH);
  delay(1000);

  digitalWrite(in2,LOW);
  delay(1000);
  digitalWrite(in2,HIGH);
  delay(1000);

  digitalWrite(in3,LOW);
  delay(1000);
  digitalWrite(in3,HIGH);
  delay(1000);
}
```

### Final Working Explanation:

1. ESP32 sets relay IN pins to **LOW to turn ON** the relay.
2. This connects the **NO and COM pins inside the relay**.
3. When NO and COM are connected, the **external 5V passes through the LED + Resistor**, lighting the LED.
4. After 1 second delay, ESP32 sets pin **HIGH to turn OFF** the relay.
5. This process repeats for all three relays.

Image :

